
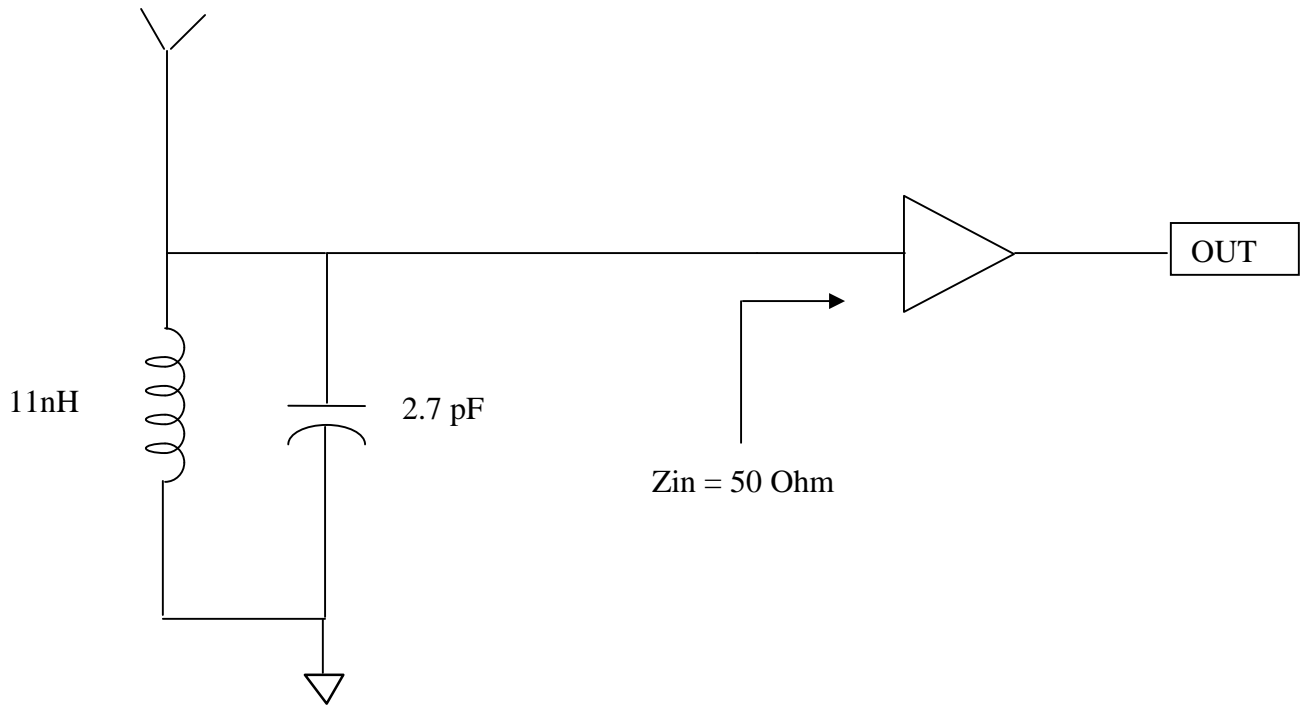


# An example in impedance matching


The problem is stated graphically below.

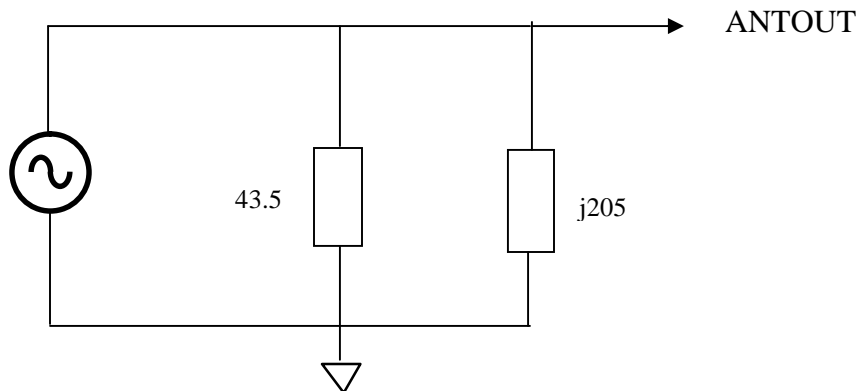


Antenna equivalent circuit at 915 Mhz.




**The complete matching problem**

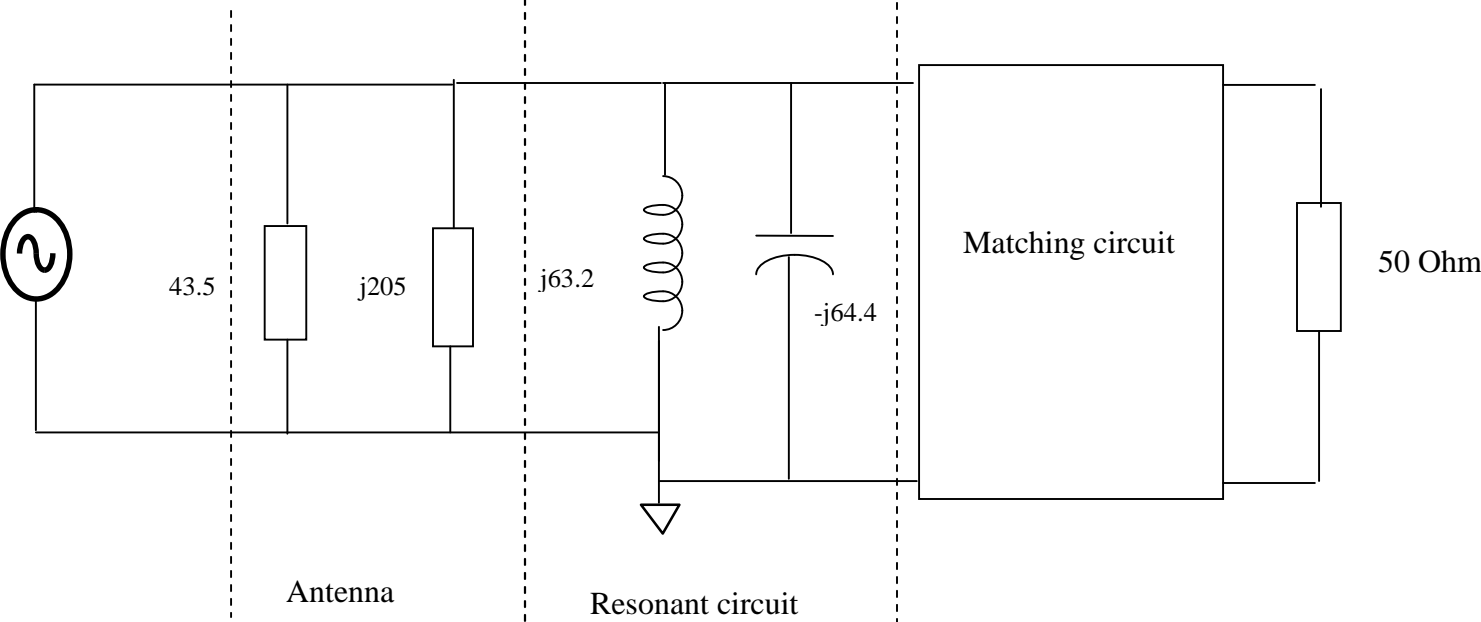

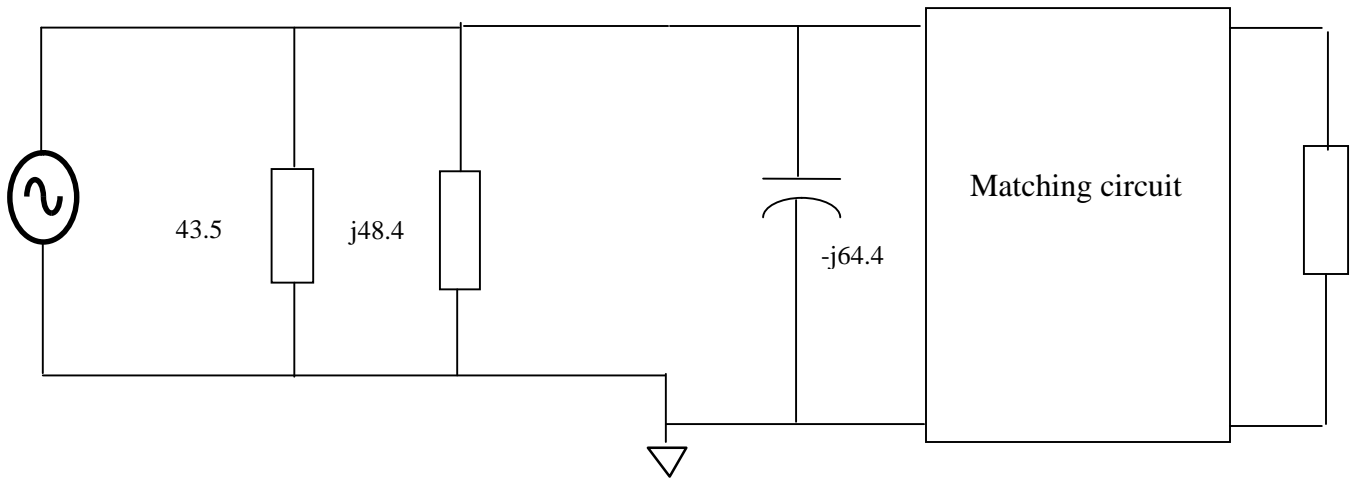**The first simplification ( combine j205 and j63.2)**



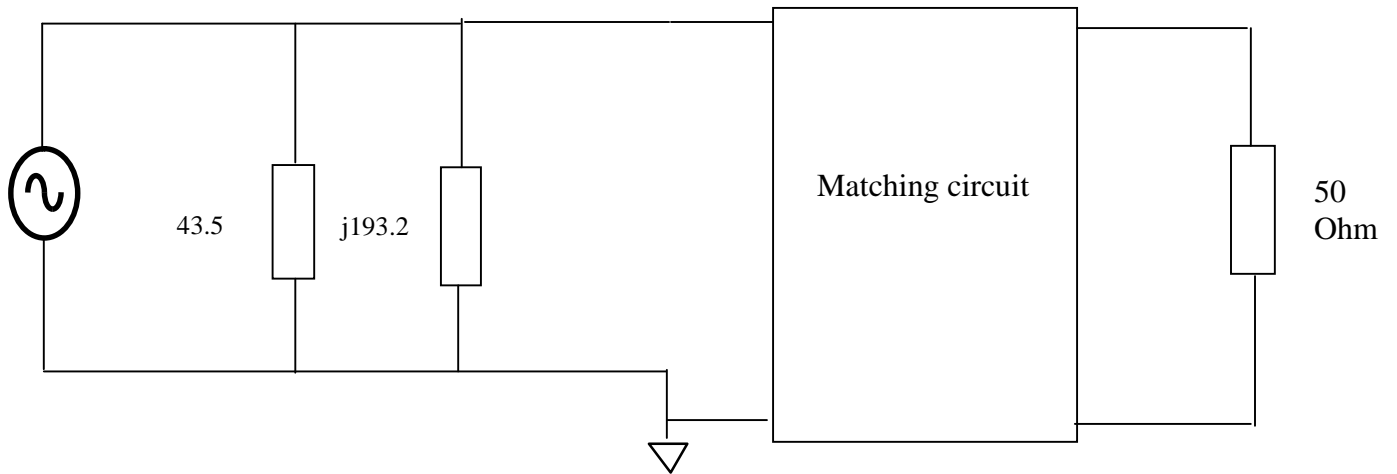**The next step – combine  $j48.4$  and  $-j64.4$**



**Now convert the input parallel circuit to series form**

The nodal Q is given by,

$$Q = \frac{193.2}{43.5} = 4.4$$


Then R series is given by,

$$R_{series} = \frac{R_{par}}{1+Q^2} = 8.0 \text{ Ohm}$$

Also Xseries is given by,


$$X_{series} = X_{par} \frac{Q^2}{1+Q^2} = 183.7 \text{ Ohm}$$

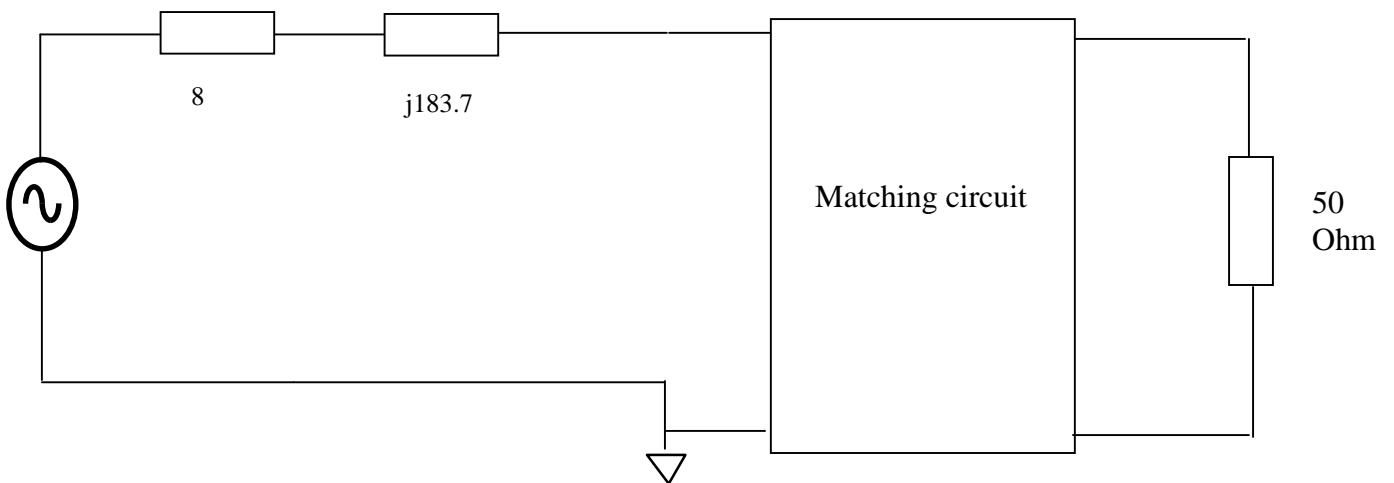This conversion is shown graphically below.


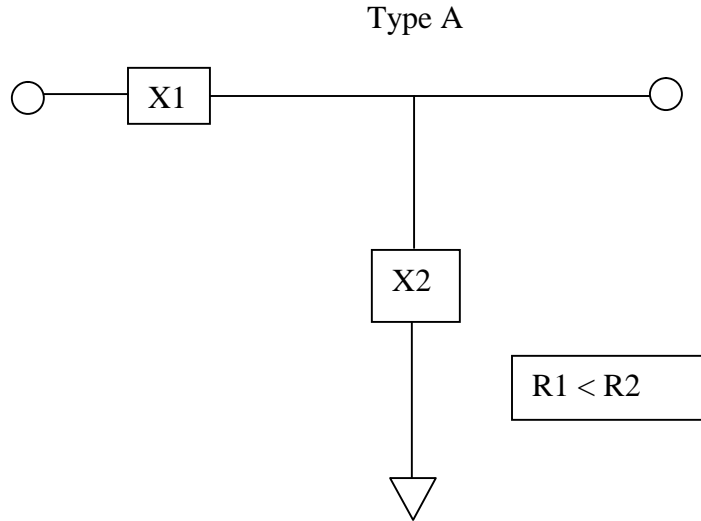
## Match 8 Ohms to 50 Ohms using a Type A network

In this case, X1 is assumed to be a capacitor and X2 is an inductor.



The formulas for the matching network are,

### Type A network:

$$X1 = \frac{\sqrt{R1R2} - R1 \cos S}{\sin S}$$

$$X2 = \frac{\sqrt{R1R2}}{\sin S}$$

Also the phase angle is defined by:

$$= \pm \cos^{-1} \sqrt{\frac{R1}{R2}} = \tan^{-1} \sqrt{\frac{R2}{R1}} - 1.0$$

The phase angle is calculated to be =  $\pm 66$  degrees

$$\cos(66) = 0.4$$


$$\sin(66) = 0.91$$

Then,

$$X2 = -j21.8 \text{ and}$$


$$X1 = j18.3$$

**Calculate the matching reactance**

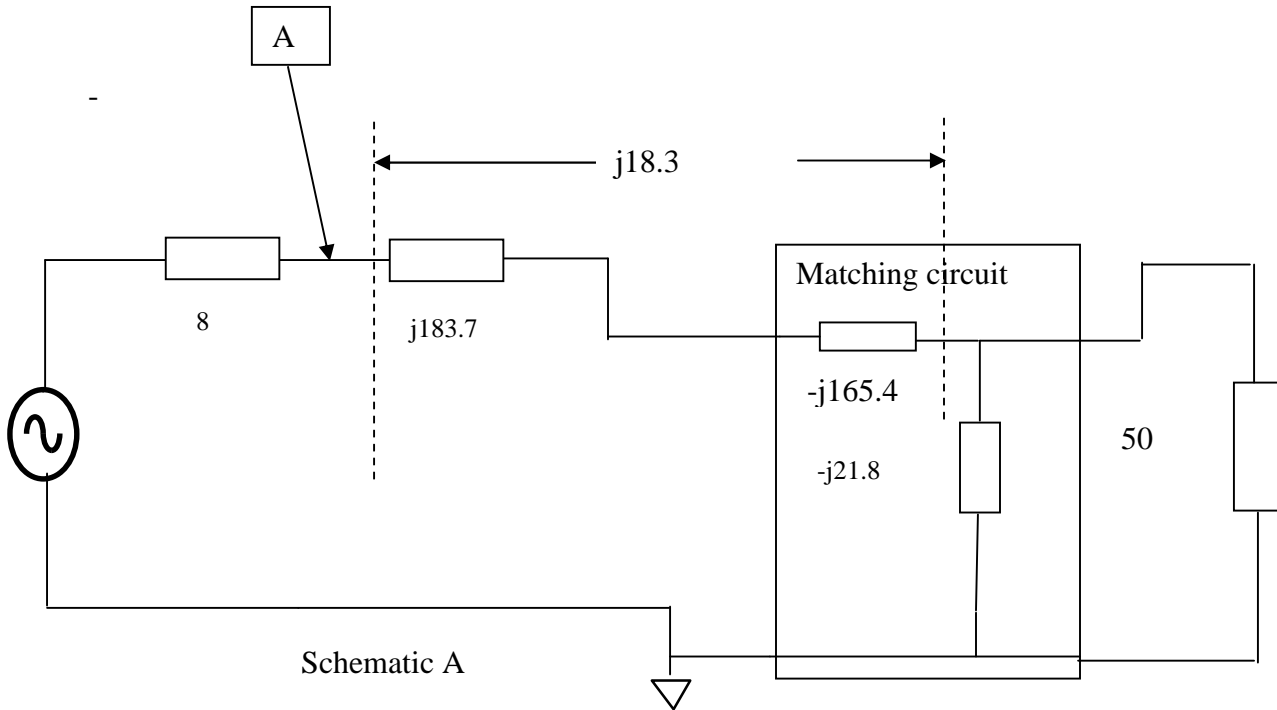

From this, the unknown reactance =  $-j165.4$  Thus the matching circuit is a TYPE A, low pass circuit with the calculated parameters.

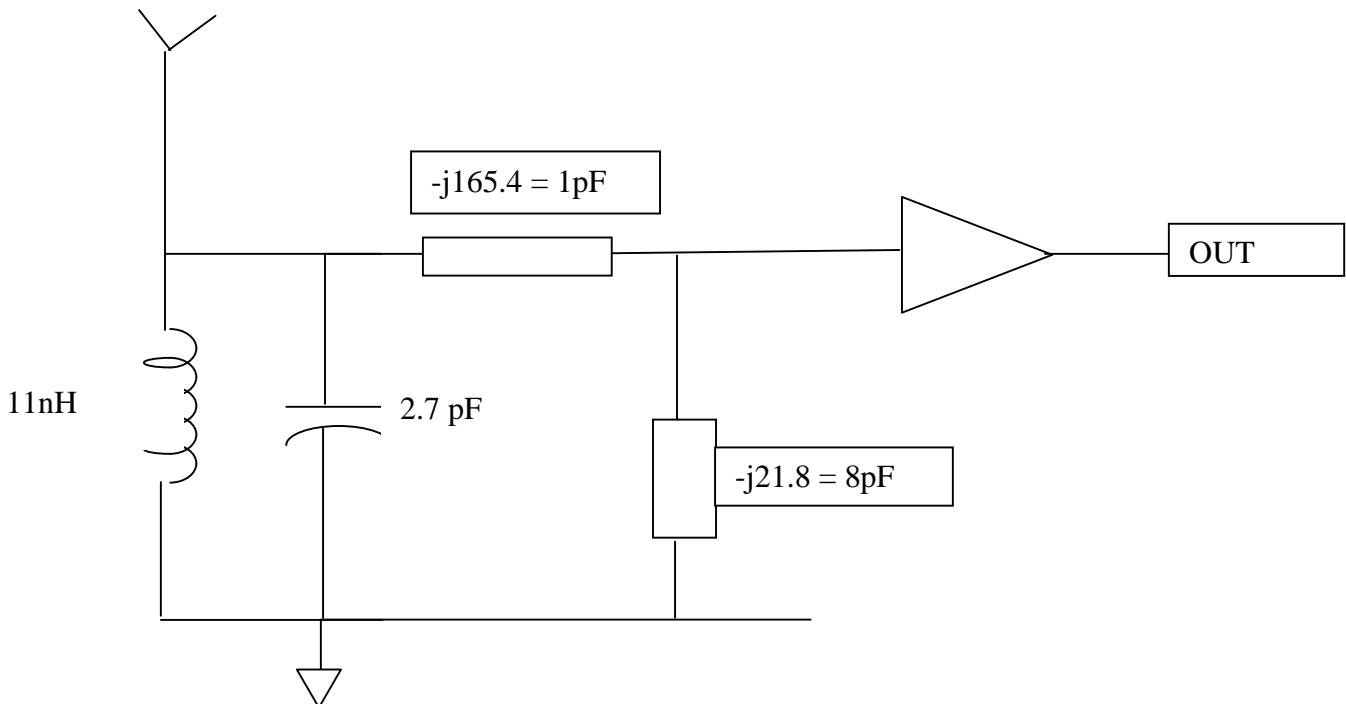So we can now show the complete circuit as ,



Now to simulate and test the design. As a check, we convert the 50 Ohm load and the 21.8 Ohm reactance to series. This is done by first calculating the Q. Which is,


$$\frac{50}{21.8} = 2.29$$

Then the series equivalent of 50 Ohm is,

$$R_{\text{series}} = 7.98$$

$$X_{\text{series}} = -j18.3$$


This converts the schematic above to,

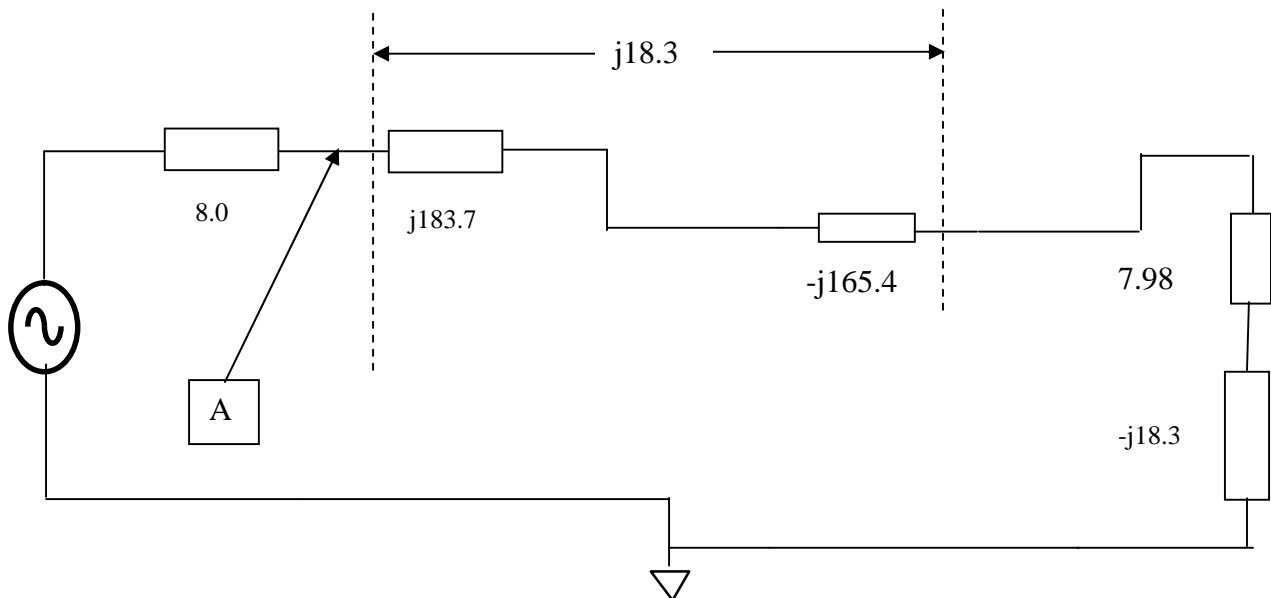

Note that the  $-j18.3$  reactance cancels the  $j18.3$  reactance leaving 7.98 Ohms matched to 8.0 Ohms at the input. Therefore the signal at point A will be attenuated by 6 dB if the match is almost perfect.

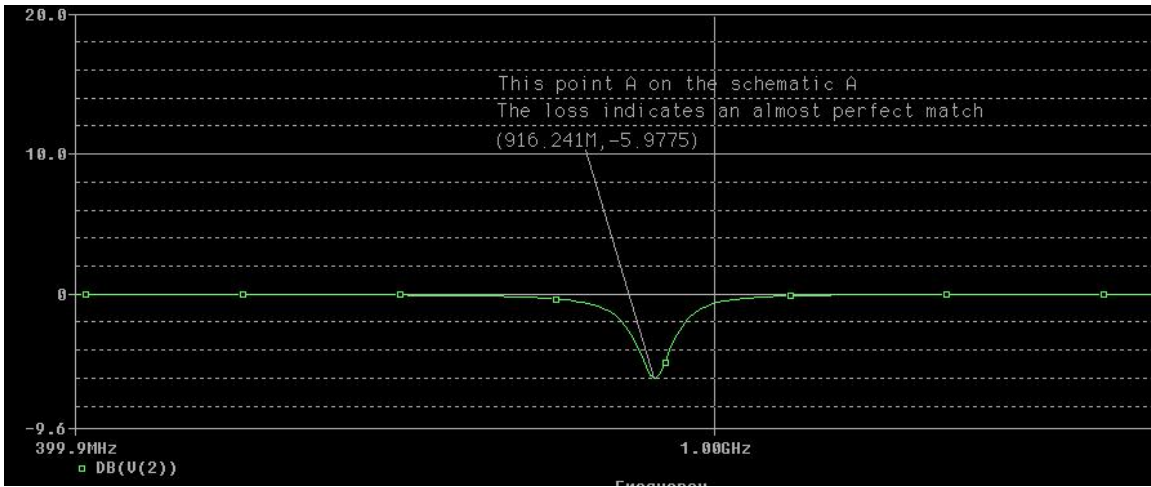A simulation of the circuit is given below, which shows the attenuation at point A on the schematic A. For a match this point should be attenuated by 6 dB at the frequency of interest, 915 Mhz.





Simulation results from PSPICE

PSPICE .cir file for the simulation

The PSPICE cir file is given below.

```
R1 in 2 8
I1 2 3 31.9n
```

```
cm1 3 out 1.05pf
cm2 out 0 7.98e-12
```

```
rload out 0 50
```

```
*****
```

```
*input signal
```

```
vin in 0 ac 1
```

```
*****
```

```
.ac oct 100 100 50g
.probe
.end
```

Note: This technical memorandum was generated by the TechTeam at Signal Processing Group Inc. Signal Processing Group Inc., designs and manufactures highly cost effective analog and RF/wireless ASICs and modules using state of the art semiconductor, PCB and packaging technology. Please contact us at [spg@signalpro.biz](mailto:spg@signalpro.biz) directly or through our website located at <http://www.signalpro.biz>.

Dated: November 29<sup>th</sup>, 2012.