


Simple L – Section and Transmission line matching techniques

February 2010

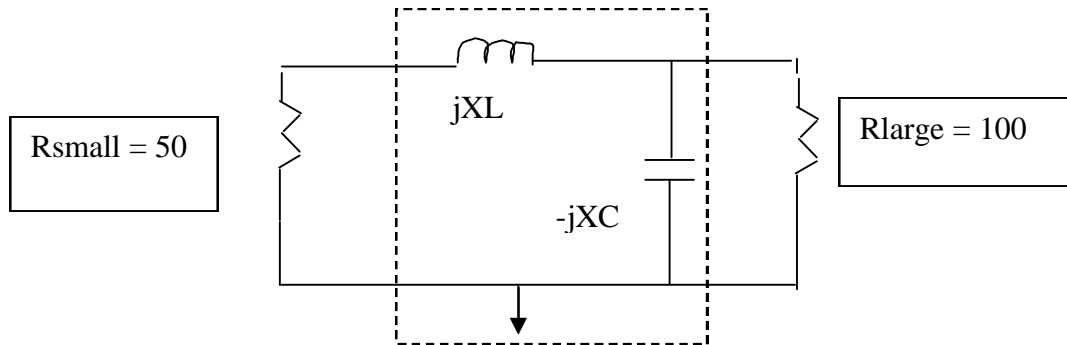1.0 Match two resistive terminations.

L – Section.

DC preserved: (Low pass section. Also the inductor and capacitor may exchange places for a high pass section. Same calculations apply)



Calculate $Q_s = Q_p = \sqrt{(R_{large}/R_{small}) - 1}$ 1.0

$Q_s = X_L/R_{small}$

$Q_p = R_{small}/X_c$

Therefore $X_L = Q_s \times R_{small}$ and $X_C = R_{small}/Q_p$ 2.0


Knowing the frequency X_L and X_C can be calculated and the values of L and C can be calculated.

Transmission line match:

Easiest matching is between real source and load.

$Z_o = \sqrt{R_{small} \cdot R_{large}}$

Ex: Here $Z_o = 10$ Ohms

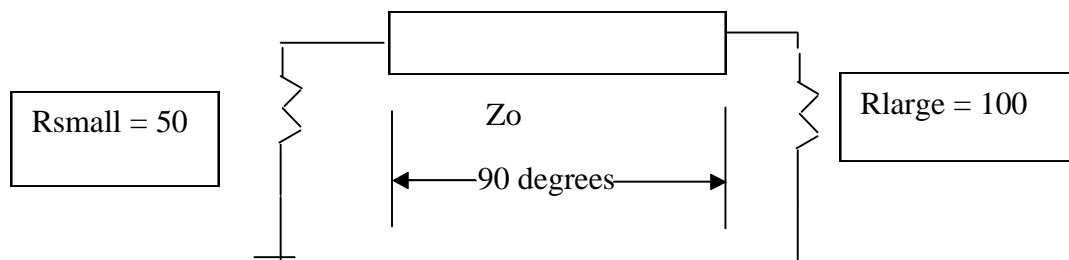

If source and load is complex then use the following formulas:

$$Z_o = \text{Sqrt}\{[(R_s^2 + X_s^2)R_L - (R_L^2 - X_L^2)R_S]/(R_S - R_L)\} \quad 3.0$$

Electrical length in degrees:

$$\text{Theta} = \text{Tan}^{-1}\{[Z_o(R_L - R_S)]/(X_S * R_L - X_L * R_S)\} \quad 4.0$$

Definition of electrical length:

$$\text{Theta} = [(\text{length of line} / \text{wavelength on the media (guide wavelength)}) * 360]. \quad 5.0$$

Note: S and L stand for source and load whether uppercase or lowercase.