

First order temperature independent resistors in analog and mixed signal IC design

In many applications of analog and mixed signal IC design, a temperature independent resistor may be required. This note describes a means to do this to a first order.

Figure 1.0 shows a series connection of two resistors which together will form the temperature independent resistor needed.

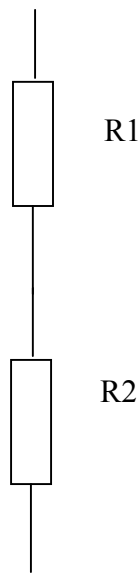


Figure 1.0

This configuration provides

$$R_{\text{total}} = R1 + R2 \quad (0)$$

Now let ,

$$R1 = R01(1+A1*dt) \quad (1)$$

$$R2 = R02(1+A2*dt) \quad (2)$$

Where A_1 , A_2 are the tempcos of the two resistors respectively and dt is the temperature differential across them.

Then the sum of the two resistors can be written:

$$R_{total} = R_{01} + R_{02} + dt(R_{01} * A_1 + R_{02} * A_2) \quad (3)$$

If,

$$R_{01} * A_1 + R_{02} * A_2 = 0.0 \quad (4)$$

Then R is temperature independent to a first order.

If A_1 is a positive tempco and A_2 is a negative tempco (a condition encountered commonly in practice) then we can write,

$$R_{01}/R_{02} = A_2/A_1 \quad (5)$$

Equation 5 and equation 3 provide the design equations for the Temperature independent resistor design.

As an example assume that a 100 Ohm temperature independent resistor is required. Lets say that poly resistors are to be used. Then a typical tempco couple may be,

$$\begin{aligned} A_1 &= 0.7E-3 \\ A_2 &= -1.2E-3 \end{aligned}$$

Using equation 5, we get:

$$R_{01} = 1.71 * R_{02} \quad (6)$$

Thus the two equations lead to:

$$R_{01} + R_{02} = 100$$

Then,

$$R_{02} = 100/2.71 \quad (7)$$

Or,

$$R02 = 36.9 \text{ Ohms} \quad (8)$$

$$R01 = 63.1 \text{ Ohms} \quad (9)$$

To cross check the results we use equation 4,

$$63.1*(0.7e-3) - 36.9*(1.2e-3) \sim 0.0$$

If necessary, slight trimming could be done using the circuit simulator to get the final values.